

Decoding the Calculator circuit

* The main idea. It depends on C_{in} , C_{out} , We are decoding the Output and displays on hexadecimal display. [C_{in} , C_{out} of the Add/subtractor circuit].

<u>C_{in}</u>	<u>C_{out}</u>	<u>Operation</u> <u>Output</u>
→ 0	1	→ Addition

Output

output is more than 15

→ 0	0	→ Addition
-----	---	------------

output is ≤ 15

→ 1	0	→ Subtraction. (Answer is negative)
-----	---	-------------------------------------

→ 1	1	→ Subtraction Answer is positive.
-----	---	-----------------------------------

decoders need to activate
→ trigger the bypass circuit
for (16, 17, 18)



→ Normal decoding circuit
for (10, 15) (0 to 15)

→ 2's complement the answer
to get the actual value.






→ Normal decoding circuit.
(0 to 15)

if (cin=0, cout=1) \rightarrow output > 15
 (21)
 { cin=0, cout=0 and 10, 11, 12, 13, 14, 15 }
 then print "1"
 cout = 1

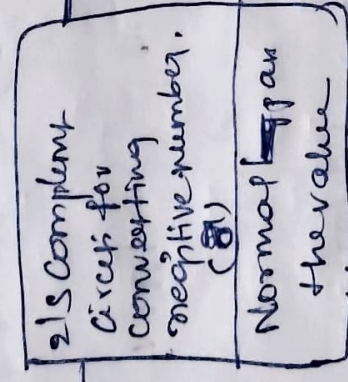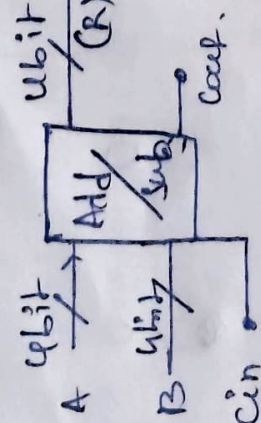if (cin=1, cout=0)
 print " - " for negative number.



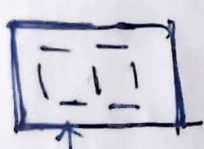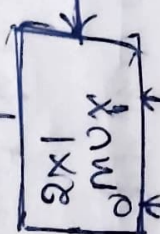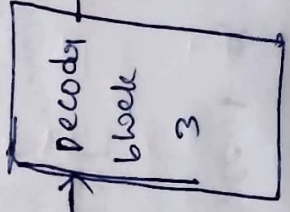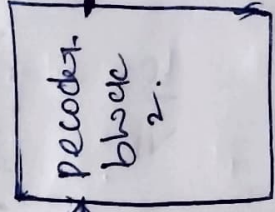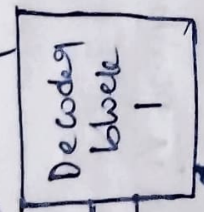if ~~cin~~
 { cin=1, cout=1 }
 (Normal pass)
 { cin=0, cout=0 }
 (2's (R)).



if (cin=0, cout=1)
 (x=1)
 { answer > 15 }
 (bypass the circuit
 i.e. $C=b$)
 and (T=1)

if.

else
 cin=0, cout=0.
 answer(n) < 15
 then { T=0 }
 { C=a }

10th phase

unit ph.

Decoder block 2:- it will just a normal decoder circuit which decodes.

0	→	0
1	→	1
2	→	2
3	→	4
⋮		
9	→	9
10	→	0
11	→	1
12	→	2
13	→	3
14	→	4
15	→	5

} 4bit data as output.


Decoder block 3:- usefully when $(x > 15)$

$$10000 (16) \rightarrow [0000] (6).$$

$$10001 (17) \rightarrow [0001] (7) \text{ (4bit data?)}$$

$$10010 (18) \rightarrow [1000] (8).$$

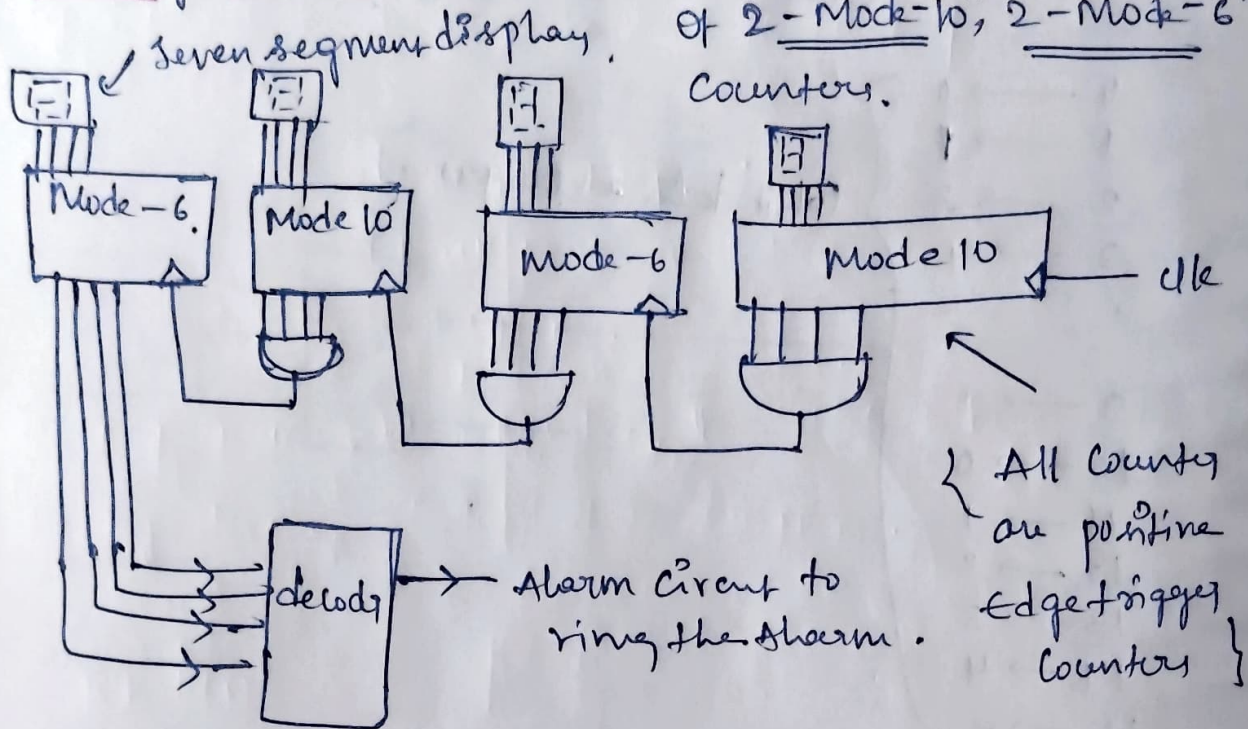Decoding Counter Circuit: — it is just a combination of "2-Mode-10", "2-Mode-6" counters.



* All AND gate will produce "1" as output where counter values = 0. Otherwise, Output of AND gate = "0".

Initial value of counters = 0, \therefore All gates AND gates initial output = 1.

xxx imp point.

Because of positive edge trigger flipflop, the counters will increment the value by "1" when a signal goes "(low to high)" at the clk input of counter
Not "(high to low)"

When counter goes,

0 to rest values, the output of

AND gate will be high to low

→ (No increment in counter value).

When the Counter will increment?

for Mode 10 Counter

When Count Value goes from 9 to "0". It means.
Output of AND gate goes [Low to high] positive edge
[trigger]

So the Corresponding Connected Counter will increment.

Similarly for Mode 6 Counter.

When the Count value goes from "5" to "0" similar thing
will happen. this is how Counter will work.
Alarm
circuit.